

## **Lab-5: Logic synthesis of an adding CPU**

**Aim:** To synthesize an adding CPU and to get the gate level netlist with timing, area, and power reports.

**EDA Tools Used:** Cadence Genus (Logic synthesis tool)

**Description:** An Adding CPU reads Load, Add, Store, and Jump instructions from its memory, and depending on the instruction it reads, loads data, performs addition, stores data into memory, or jumps to another memory location. The Adding CPU has a main register called AC (accumulator). The Load instruction directs the machine to load the addressed data from the memory into AC. The Store instruction causes contents of AC to be written into the addressed location in the memory. The operand of the Add instruction is immd (immediate). This instruction adds immd to the present contents of AC and puts the result back into AC. The Jump instruction loads the 6-bit address into the program counter of our machine, causing the next instruction to be fetched from this address.

### **Procedure:**

1. Copy the fast.lib and slow.lib files into the folder where (.v) files are located.
2. Create a Synopsys design constraint file (.SDC file) by entering the design constraints required for the synthesis.

## Lab-5: Logic synthesis of an adding CPU

```
File Edit View Search Tools Documents Help
AC.v addingCPU.sdc addingCPU.tcl AddingCPU.v ALU.v Controller.v DataPath.v IR.v PC.v
1 create_clock -name CLK_100M -period 10 -waveform {0 5} [get_ports "clk"]
2
3 set_clock_transition -rise 0.1 [ get_clocks "CLK_100M" ]
4
5 set_clock_transition -fall 0.1 [ get_clocks "CLK_100M" ]
6
7 set_clock_uncertainty 0.01 [ get_ports "clk" ]
8
9
10 set_input_delay -max 1.0 [get_ports "clk"] -clock CLK_100M
11
12 set_input_delay -max 1.0 [get_ports "reset"] -clock CLK_100M
13
14 set_input_delay -max 1.0 [get_ports "data_bus"] -clock CLK_100M
15
16 set_output_delay -max 1.0 [get_ports "data_bus"] -clock CLK_100M
17
18
19 set_output_delay -max 1.0 [get_ports "adr_bus"] -clock CLK_100M
20
21 set_output_delay -max 1.0 [get_ports "rd_mem"] -clock CLK_100M
22
23 set_output_delay -max 1.0 [get_ports "wr_mem"] -clock CLK_100M
24
25
26
```

3. Create a (.tcl) file containing all the commands for performing the logic synthesis. Synthesis effort can be medium or high.

```
File Edit View Search Tools Documents Help
AC.v addingCPU.sdc addingCPU.tcl AddingCPU.v ALU.v Controller.v DataPath.v IR.v PC.v
1 set attr library slow.lib
2 read_hdl { AddingCPU.v DataPath.v Controller.v IR.v PC.v AC.v ALU.v }
3
4 elaborate
5
6 read_sdc addingCPU.sdc
7 synthesize -to_mapped -effort medium
8 write_hdl > addingCPU_netlist.v
9
10 write_sdc > addingCPU_constraint_created.sdc
11 write_sdf > addingCPU_sdf_created.sdf
12
13 gui_show
14
15 report_timing > addingCPU_timing_created.rep
16 report_area > addingCPU_area_created.rep
17 report_power > addingCPU_power_created.rep
18 report_gates > addingCPU_gates_created.rep
19 report_qor > addingCPU_quality_created.rep
20
```

4. Invoke the C shell and launch the Genus tool by entering the below commands.

## Lab-5: Logic synthesis of an adding CPU

5. Execute the commands in the (.tcl file) by entering **source addingCPU.tcl** command in the command line window.
6. Check for the area, timing and power reports generated in the respective adding CPU folder. Also check the gate level netlist generated in the Genus synthesis solution window.

### Verilog Programs:

#### //Verilog Program of top module of adding CPU

```
File Edit View Search Tools Documents Help
AC.v x addingCPU.sdc x addingCPU.tcl x AddingCPU.v x ALU.v x Controller.v x DataPath.v x IR.v x PC.v x
1 module AddingCPU(input reset,clk, output [5:0]adr_bus,output rd_mem, wr_mem, inout [7:0]data_bus);
2
3 wire ir_on_adr, pc_on_adr,dbus_on_data,data_on_dbus,ld_ir,ld_ac,ld_pc,inc_pc,clr_pc,pass,add,alu_on_dbus;
4 wire [1:0]op_code;
5
6 Controller cu (reset,clk,op_code,rd_mem,wr_mem,ir_on_adr,pc_on_adr,dbus_on_data,data_on_dbus,ld_ir,
7 ld_ac,ld_pc,inc_pc,clr_pc,pass,add,alu_on_dbus);
8
9 DataPath dp (ir_on_adr,pc_on_adr,dbus_on_data,data_on_dbus,ld_ir,ld_ac,ld_pc,inc_pc,clr_pc,pass,add,
10 alu_on_dbus,clk,adr_bus,op_code,data_bus);
11
12 endmodule
```

# Lab-5: Logic synthesis of an adding CPU

## //Verilog Program of the Controller

```
File Edit View Search Tools Documents Help
AC.v addingCPU.sdc addingCPU.tcl AddingCPU.v ALU.v Controller.v DataPath.v IR.v PC.v
1 `define Reset 2'b00
2 `define Fetch 2'b01
3 `define Decode 2'b10
4 `define Execute 2'b11
5 module Controller ( input reset, clk, input [1:0] op_code,
6                     output reg rd_mem, wr_mem, ir_on_adr, pc_on_adr, dbus_on_data, data_on_dbus, ld_ir, ld_ac, ld_pc, inc_pc, clr_pc, pass, add, alu_on_dbus);
7
8 reg [1:0] present_state, next_state;
9 always @(posedge clk)
10 if( reset ) present_state <= `Reset;
11 else present_state <= next_state;
12
13 always @( present_state or reset ) begin : Combinational
14 rd_mem=1'b0; wr_mem=1'b0; ir_on_adr=1'b0; pc_on_adr=1'b0;
15 dbus_on_data=1'b0; data_on_dbus=1'b0; ld_ir=1'b0;
16 ld_ac=1'b0; ld_pc=1'b0; inc_pc=1'b0; clr_pc=1'b0;
17 pass=1'b0; add=1'b0; alu_on_dbus=1'b0;
18
19 case ( present_state )
20
21 `Reset : begin next_state = reset ? `Reset : `Fetch; clr_pc = 1'b1;
22           end // End `Reset
23 `Fetch : begin next_state = `Decode; pc_on_adr = 1'b1; rd_mem = 1'b1; data_on_dbus = 1'b1; ld_ir = 1'b1; inc_pc = 1'b1;
24           end // End `Fetch
25 `Decode : next_state = `Execute; // End `Decode
26 `Execute : begin next_state = `Fetch;
27
28 case( op_code )
29
30     2'b00: begin ir_on_adr = 1'b1; rd_mem = 1'b1; data_on_dbus = 1'b1; ld_ac = 1'b1;
31             end
32     2'b01: begin pass = 1'b1; ir_on_adr = 1'b1; alu_on_dbus = 1'b1; dbus_on_data = 1'b1; wr_mem = 1'b1;
33             end
34     2'b10: ld_pc = 1'b1;
35     2'b11: begin add = 1'b1; alu_on_dbus = 1'b1; ld_ac = 1'b1;
36             end
37
38 endcase
39 end // End `Execute
40 default : next_state = `Reset;
41 endcase
42 end
43
44 endmodule
```

## //Verilog Program of DataPath

```
File Edit View Search Tools Documents Help
AC.v addingCPU.sdc addingCPU.tcl AddingCPU.v ALU.v Controller.v DataPath.v IR.v PC.v
1 module DataPath ( input ir_on_adr, pc_on_adr, dbus_on_data,
2                   data_on_dbus, ld_ir, ld_ac, ld_pc,
3                   inc_pc, clr_pc, pass, add, alu_on_dbus, clk,
4                   output [5:0] adr_bus,
5                   output [1:0] op_code,
6                   inout [7:0] data_bus );
7 wire [7:0] dbus, ir_out, a_side, alu_out;
8 wire [5:0] pc_out;
9 IR ir ( dbus, ld_ir, clk, ir_out );
10 PC pc ( ir_out[5:0], ld_pc, inc_pc, clr_pc, clk, pc_out );
11 AC ac ( dbus, ld_ac, clk, a_side );
12 ALU alu ( a_side, {2'b00, ir_out[5:0]}, pass, add, alu_out );
13
14 assign adr_bus = ir_on_adr ? ir_out[5:0] : 6'bzz_zzzz;
15 assign adr_bus = pc_on_adr ? pc_out : 6'bzz_zzzz;
16 assign dbus = alu_on_dbus ? alu_out : 8'bzzzz_zzzz;
17 assign data_bus = dbus_on_data ? dbus : 8'bzzzz_zzzz;
18 assign dbus = data_on_dbus ? data_bus : 8'bzzzz_zzzz;
19 assign op_code = ir_out[7:6];
20 endmodule
21
```

## Lab-5: Logic synthesis of an adding CPU

### //Verilog Program of IR

```
File Edit View Search Tools Documents Help
AC.v x addingCPU.sdc x addingCPU.tcl x AddingCPU.v x ALU.v x Controller.v x DataPath.v x IR.v x PC.v x
1 module IR(data_in,load,clk,data_out);
2 input [7:0] data_in;
3 input clk,load;
4 output reg [7:0]data_out;
5 always@(posedge clk)
6 begin
7 if(load)
8 begin
9 data_out<=data_in;
10 end
11 endmodule
```

### //Verilog Program of PC

```
File Edit View Search Tools Documents Help
AC.v x addingCPU.sdc x addingCPU.tcl x AddingCPU.v x ALU.v x Controller.v x DataPath.v x IR.v x PC.v x
1 module PC(data_in,load,clk,clr,inc,data_out);
2 input [5:0] data_in;
3 input load,clk,clr,inc;
4 output reg [5:0]data_out;
5 always@(posedge clk)
6 begin
7 if(clr) data_out<=6'b000_000;
8 else if (load) data_out<=data_in;
9 else if (inc) data_out<=data_out +1;
10 end
11 endmodule
```

### //Verilog Program of AC

```
File Edit View Search Tools Documents Help
AC.v x addingCPU.sdc x addingCPU.tcl x AddingCPU.v x ALU.v x Controller.v x DataPath.v x IR.v x PC.v x
1 module AC(input [7:0] data_in, input load,clk,output reg[7:0] data_out);
2 always@(posedge clk)
3 if(load) data_out <= data_in;
4 endmodule
```

## Lab-5: Logic synthesis of an adding CPU


## //Verilog Program of the ALU

File Edit View Search Tools Documents Help

AC.v addingCPU.sdc addingCPU.tcl AddingCPU.v ALU.v Controller.v DataPath.v IR.v PC.v



```
1 module ALU (input [7:0] a,b, input pass, add, output reg [7:0] alu_out);
2 always@(a or b or pass or add)
3 if(pass) alu_out = a;
4 else if (add) alu_out = a+b;
5 else alu_out =0;
6 endmodule
```

### Gate level Netlist:

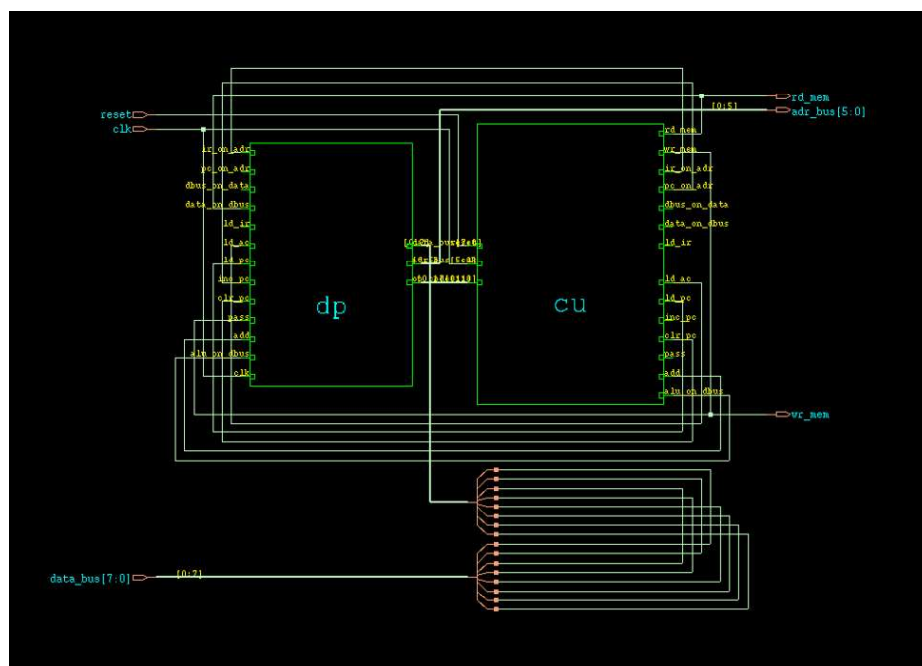


 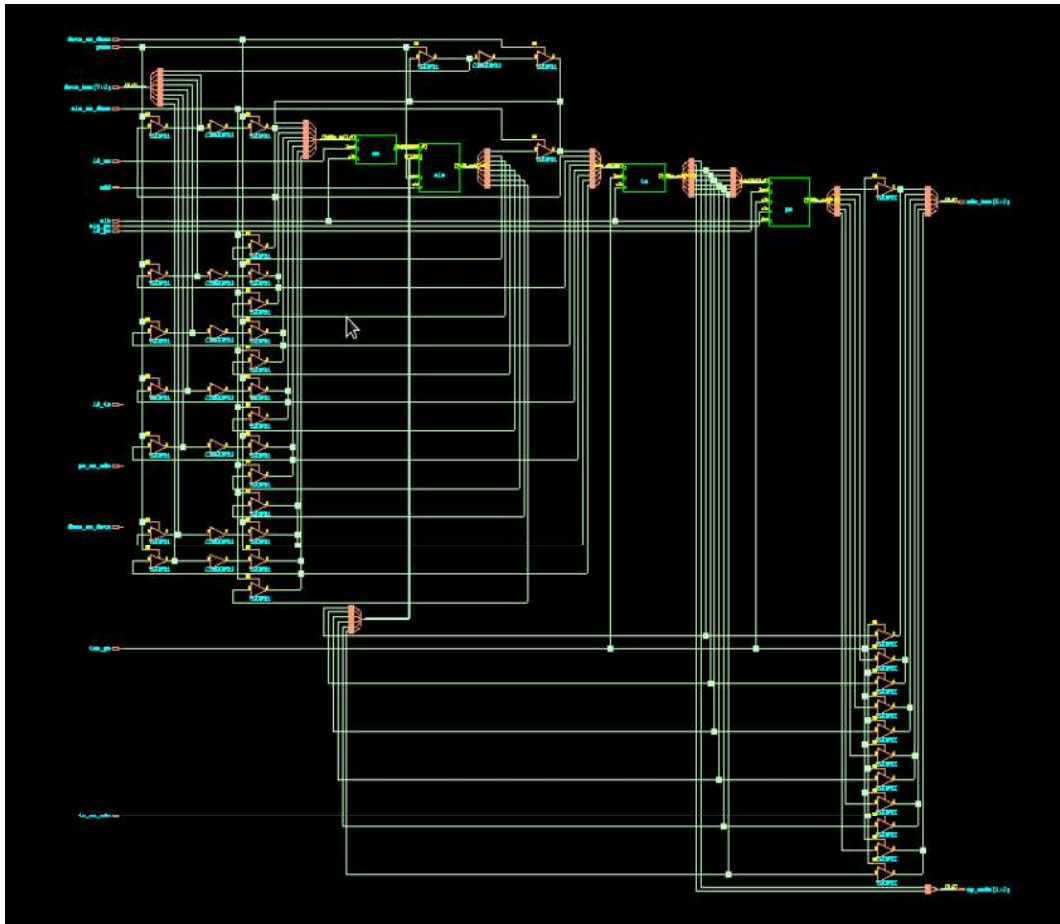
## Lab-5: Logic synthesis of an adding CPU



## Lab-5: Logic synthesis of an adding CPU

### Observations:

Synthesis effort: Medium

#### a) addingCPU\_netlist\_created file

```
addingCPU_netlist.v
// Generated by Cadence Genus(TM) Synthesis Solution 17.21-s010.1
// Generated on: May  4 2023 12:35:49 IST (May  4 2023 07:05:49 UTC)
// Verification Directory fv/AddingCPU

module Controller(reset, clk, op_code, rd_mem, wr_mem, ir_on_adr,
pc_on_adr, dbus_on_data, data_on_dbus, ld_ir, ld_ac, ld_pc,
inc_pc, clr_pc, pass, add, alu_on_dbus);
input reset, clk;
input [1:0] op_code;
output rd_mem, wr_mem, ir_on_adr, pc_on_adr, dbus_on_data,
data_on_dbus, ld_ir, ld_ac, ld_pc, inc_pc, clr_pc, pass, add,
alu_on_dbus;
wire reset, clk;
wire [1:0] op_code;
wire rd_mem, wr_mem, ir_on_adr, pc_on_adr, dbus_on_data,
data_on_dbus, ld_ir, ld_ac, ld_pc, inc_pc, clr_pc, pass, add,
alu_on_dbus;
wire [1:0] present_state;
wire n_0, n_1, n_2, n_3, n_4, n_5, n_6, n_7;
wire n_8;
OAI21X1 g309(.A0 (op_code[0]), .A1 (n_7), .B0 (n_8), .Y (ld_ac));
AND2X1 g310(.A (present_state[0]), .B (n_6), .Y (rd_mem));
NOR2BX1 g311(.AN (alu_on_dbus), .B (op_code[1]), .Y (wr_mem));
INVXL g312(.A (add), .Y (n_8));
AND2X1 g314(.A (op_code[1]), .B (alu_on_dbus), .Y (add));
NOR2BX1 g315(.AN (op_code[0]), .B (n_5), .Y (alu_on_dbus));
INVXL g316(.A (ir_on_adr), .Y (n_7));
OAI21X1 g317(.A0 (op_code[0]), .A1 (op_code[1]), .B0
(present_state[1]), .Y (n_6));
NOR2XL g318(.A (op_code[1]), .B (n_5), .Y (ir_on_adr));
NAND2XL g319(.A (present_state[1]), .B (present_state[0]), .Y (n_5));
NOR2BXL g320(.AN (present_state[0]), .B (present_state[1]), .Y
(pc_on_adr));
NOR2XL g321(.A (present_state[1]), .B (present_state[0]), .Y
(clr_pc));
NOR3BX1 g2(.AN (op_code[1]), .B (op_code[0]), .C (n_5), .Y (ld_pc));
DFFQX1 \present_state reg[0] (.CK (clk), .D (n_4), .Q
(present_state[0]));
DFFQX1 \present_state reg[1] (.CK (clk), .D (n_3), .Q
(present_state[1]));
NOR2XL g185(.A (reset), .B (n_1), .Y (n_4));
NOR2XL g186(.A (reset), .B (n_2), .Y (n_3));
ADDHXL g187(.A (present_state[0]), .B (n_0), .C0 (n_1), .S (n_2));
CLKINVLX1 g188(.A (present_state[1]), .Y (n_0));
endmodule

addingCPU_netlist.v
module DataPath(ir_on_adr, pc_on_adr, dbus_on_data, data_on_dbus,
ld_ir, ld_ac, ld_pc, inc_pc, clr_pc, pass, add, alu_on_dbus, clk,
adr_bus, op_code, data_bus);
input ir_on_adr, pc_on_adr, dbus_on_data, data_on_dbus, ld_ir, ld_ac,
ld_pc, inc_pc, clr_pc, pass, add, alu_on_dbus, clk;
output [5:0] adr_bus;
output [1:0] op_code;
inout [7:0] data_bus;
wire ir_on_adr, pc_on_adr, dbus_on_data, data_on_dbus, ld_ir, ld_ac,
ld_pc, inc_pc, clr_pc, pass, add, alu_on_dbus, clk;
wire [5:0] adr_bus;
wire [1:0] op_code;
wire [7:0] data_bus;
wire [7:0] a_side;
wire [7:0] ir_out;
wire [7:0] alu_out;
wire [5:0] pc_out;
wire UNCONNECTED_HIER_Z, UNCONNECTED_HIER_Z0, n_1, n_2, n_3, n_4,
n_5, n_6;
wire n_7, n_8;
AC ac(dbus, ld_ac, clk, a_side);
ALU alu(a_side, {UNCONNECTED_HIER_Z0, UNCONNECTED_HIER_Z,
ir_out[5:0]}, pass, add, alu_out);
IR ir(dbus, inc_pc, clk, {op_code, ir_out[5:0]});
PC pc(ir_out[5:0], ld_pc, inc_pc, clr_pc, clk, pc_out);
CLKBUF2X2 cdn_loop_breaker51(.A (data_bus[6]), .Y (n_7));
CLKBUF2X2 cdn_loop_breaker52(.A (data_bus[5]), .Y (n_6));
CLKBUF2X2 cdn_loop_breaker53(.A (data_bus[4]), .Y (n_5));
CLKBUF2X2 cdn_loop_breaker54(.A (data_bus[3]), .Y (n_4));
CLKBUF2X2 cdn_loop_breaker55(.A (data_bus[2]), .Y (n_3));
CLKBUF2X2 cdn_loop_breaker56(.A (data_bus[1]), .Y (n_2));
CLKBUF2X2 cdn_loop_breaker57(.A (data_bus[0]), .Y (n_1));
TBUFXL g1(.A (ir_out[5]), .OE (ir_on_adr), .Y (adr_bus[5]));
TBUFXL g23(.A (ir_out[4]), .OE (ir_on_adr), .Y (adr_bus[4]));
TBUFXL g25(.A (ir_out[2]), .OE (ir_on_adr), .Y (adr_bus[2]));
TBUFXL g26(.A (ir_out[1]), .OE (ir_on_adr), .Y (adr_bus[1]));
TBUFXL g24(.A (ir_out[3]), .OE (ir_on_adr), .Y (adr_bus[3]));
TBUFXL g6(.A (ir_out[0]), .OE (ir_on_adr), .Y (adr_bus[0]));
TBUFXL g27(.A (pc_out[5]), .OE (inc_pc), .Y (adr_bus[5]));
TBUFXL g2(.A (pc_out[4]), .OE (inc_pc), .Y (adr_bus[4]));
TBUFXL g29(.A (pc_out[2]), .OE (inc_pc), .Y (adr_bus[2]));
TBUFXL g30(.A (pc_out[1]), .OE (inc_pc), .Y (adr_bus[1]));
TBUFXL g28(.A (pc_out[3]), .OE (inc_pc), .Y (adr_bus[3]));
TBUFXL g31(.A (pc_out[0]), .OE (inc_pc), .Y (adr_bus[0]));
TBUFXL g39(.A (dbus[5]), .OE (pass), .Y (data_bus[5]));
TBUFXL g38(.A (dbus[6]), .OE (pass), .Y (data_bus[6]));
TBUFXL g37(.A (dbus[7]), .OE (pass), .Y (data_bus[7]));
TBUFXL g41(.A (dbus[2]), .OE (pass), .Y (data_bus[2]));
TBUFXL g43(.A (dbus[0]), .OE (pass), .Y (data_bus[0]));
TBUFXL g42(.A (dbus[1]), .OE (pass), .Y (data_bus[1]));
TBUFXL g4(.A (dbus[4]), .OE (pass), .Y (data_bus[4]));
TBUFXL g40(.A (dbus[3]), .OE (pass), .Y (data_bus[3]));
TBUFXL g7(.A (alu_out[1]), .OE (alu_on_dbus), .Y (dbus[1]));
TBUFXL g5(.A (n_4), .OE (data_on_dbus), .Y (dbus[3]));
TBUFXL g46(.A (n_6), .OE (data_on_dbus), .Y (dbus[5]));
TBUFXL g4(.A (n_3), .OE (data_on_dbus), .Y (dbus[2]));
TBUFXL g36(.A (alu_out[2]), .OE (alu_on_dbus), .Y (dbus[2]));
TBUFXL g3(.A (alu_out[5]), .OE (alu_on_dbus), .Y (dbus[5]));
TBUFXL g49(.A (n_2), .OE (data_on_dbus), .Y (dbus[1]));
TBUFXL g44(.A (n_8), .OE (data_on_dbus), .Y (dbus[7]));
TBUFXL g45(.A (n_7), .OE (data_on_dbus), .Y (dbus[6]));
```



## Lab-5: Logic synthesis of an adding CPU

### b) addingCPU\_Constraint\_created file

```
addingCPU_constraint_created.sdc
# =====
# Created by Genus(TM) Synthesis Solution 17.21-s010_1 on Thu May 04 12:35:49 IST 2023
# =====

set sdc_version 2.0

set units -capacitance 1000.0fF
set units -time 1000.0ps

# Set the current design
current_design AddingCPU

create_clock -name "CLK_100M" -period 10.0 -waveform {0.0 5.0} [get_ports clk]
set_clock_transition 0.1 [get_clocks CLK_100M]
set_clock_gating_check -setup 0.0

set_input_delay -clock [get_clocks CLK_100M] -network_latency_included -add_delay -rise -min 0.0 [get_ports clk]
set_input_delay -clock [get_clocks CLK_100M] -clock_fall -network_latency_included -add_delay -fall -min 0.0 [get_ports clk]
set_input_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports clk]
set_input_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports reset]
set_input_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[7]}]
set_input_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[6]}]
set_input_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[5]}]
set_input_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[4]}]
set_input_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[3]}]
set_input_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[2]}]
set_input_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[1]}]
set_input_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[0]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[7]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[6]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[5]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[4]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[3]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[2]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[1]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {data_bus[0]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {adr_bus[5]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {adr_bus[4]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {adr_bus[3]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {adr_bus[2]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {adr_bus[1]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {adr_bus[0]}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {rd_mem}]
set_output_delay -clock [get_clocks CLK_100M] -add_delay -max 1.0 [get_ports {wr_mem}]

set_wire_load_mode "enclosed"
set_dont_use [get_lib_cells slow/HOLDX1]
set_clock_uncertainty -setup 0.01 [get_ports clk]
set_clock_uncertainty -hold 0.01 [get_ports clk]
```

### c) addingCPU\_sdf\_created file

```
addingCPU_sdf_created.sdf
(DELAYFILE
  (SDPVERSION "0VI 3.0")
  (DESIGN "AddingCPU")
  (DATE "Thu May 04 12:35:49 IST 2023")
  (VENDOR "Cadence, Inc.")
  (PROGRAM "Genus(TM) Synthesis Solution")
  (VERSION "17.21-s010_1")
  (DIVIDER ".")
  (VOLTAGE "1.0V")
  (PROCESS "1.0")
  (TEMPERATURE "125.0")
  (TIMESCALE "1ps")
  (CELL
    (CELLTYPE "OAI21X1")
    (INSTANCE cu.g309)
    (DELAY
      (ABSOLUTE
        (PORT A0 (:::0.0))
        (PORT A1 (:::0.0))
        (PORT B0 (:::0.0))
        (IOPATH A0 Y (:::402) (:::336))
        (IOPATH B0 Y (:::213) (:::321))
        (IOPATH A1 Y (:::419) (:::327))
      )
    )
  )
  (CELL
    (CELLTYPE "AND2X1")
    (INSTANCE cu.g310)
    (DELAY
      (ABSOLUTE
        (PORT A (:::0.0))
        (PORT B (:::0.0))
        (IOPATH A Y (:::295) (:::236))
        (IOPATH B Y (:::287) (:::221))
      )
    )
  )
  (CELL
    (CELLTYPE "NOR2BX1")
    (INSTANCE cu.g311)
    (DELAY
      (ABSOLUTE
        (PORT AN (:::0.0))
        (PORT B (:::0.0))
        (IOPATH B Y (:::548) (:::257))
        (IOPATH AN Y (:::638) (:::351))
      )
    )
  )
  (CELL
    (CELLTYPE "INVXL")
    (INSTANCE cu.g312)
    (DELAY
      (ABSOLUTE
        (PORT A (:::0.0))
        (IOPATH A Y (:::78) (:::68))
      )
    )
  )
  (CELL
    (CELLTYPE "AND3V1")
    (INSTANCE cu.g313)
    (DELAY
      (ABSOLUTE
        (PORT A0 (:::0.0))
        (PORT A1 (:::0.0))
        (PORT A2 (:::0.0))
        (IOPATH A0 Y (:::402) (:::336))
        (IOPATH A1 Y (:::213) (:::321))
        (IOPATH A2 Y (:::419) (:::327))
      )
    )
  )
)
```

```

addingCPU_area_created.rep
=====
Generated by:      Genus(TM) Synthesis Solution 17.21-s010_1
Generated on:      May 04 2023 12:35:50 pm
Module:           AddingCPU
Technology library: slow
Operating conditions: slow (balanced_tree)
Wireload mode:    enclosed
Area mode:        timing library
=====

Instance  Module      Cell Count  Cell Area  Net Area  Total Area  Wireload
-----
AddingCPU
  dp      DataPath    152    1224.664    0.000    1224.664    <none> (D)
    pc    PC         30     215.716    0.000     215.716    <none> (D)
    alu   ALU        43     214.960    0.000     214.960    <none> (D)
    ir    IR         8      163.490    0.000     163.490    <none> (D)
    ac    AC         8      163.490    0.000     163.490    <none> (D)
    cu    Controller  19     183.695    0.000     183.695    <none> (D)

(D) = wireload is default in technology library

```

## Lab-5: Logic synthesis of an adding CPU

f) addingCPU \_power\_created file

addingCPU_power_created.rep				
Generated by: Genus(TM) Synthesis Solution 17.21-s010_1				
Generated on: May 04 2023 12:35:50 pm				
Module: AddingCPU				
Technology library: slow				
Operating conditions: slow (balanced_tree)				
Wireload mode: enclosed				
Area mode: timing library				
		Leakage	Dynamic	Total
Instance	Cells	Power(nW)	Power(nW)	Power(nW)
AddingCPU	152	6669.930	77398.874	84068.804
dp	133	6137.071	65606.163	71743.234
pc	30	1167.830	9818.709	10986.539
ac	8	1090.048	18564.195	19654.243
ir	8	1090.048	20632.354	21722.402
alu	43	887.626	5009.390	5897.015
cu	19	532.858	8834.186	9367.045

g) addingCPU \_gates\_created file

addingCPU_gates_created.rep			
Generated by: Genus(TM) Synthesis Solution 17.21-s010_1			
Generated on: May 04 2023 12:35:50 pm			
Module: AddingCPU			
Technology library: slow			
Operating conditions: slow (balanced_tree)			
Wireload mode: enclosed			
Area mode: timing library			
Gate	Instances	Area	Library
ADDFX1	2	39.359	slow
ADDHXL	1	12.110	slow
AND2X1	2	9.083	slow
ANDXX1	10	75.690	slow
A0I21X1	7	31.790	slow
A0I21XL	1	4.541	slow
A0I2B81X1	1	6.055	slow
CLKBUF2X1	8	36.331	slow
CLKINVX1	2	4.541	slow
CLKXOR2X1	1	8.326	slow
DFFQX1	8	127.159	slow
INVL	2	4.541	slow
INVL	6	13.624	slow
MXI2XL	1	6.055	slow
NAND2BX1	1	4.541	slow
NAND2BXL	4	18.166	slow
NAND2XL	12	36.331	slow
NOR2BX1	2	9.083	slow
NOR2BXL	2	9.083	slow
NOR2XL	12	36.331	slow
NOR3BX1	1	6.055	slow
OAI21X1	5	22.707	slow
OAI21XL	5	22.707	slow
OAI31X1	1	6.055	slow
OAI32X1	3	20.436	slow
SOPFQX1	16	326.981	slow
TBUF2X1	24	217.987	slow
TBUFXL	12	108.994	slow
total	152	1224.664	
Type	Instances	Area	Area %
sequential	24	454.140	37.1
inverter	10	22.707	1.9
buffer	8	36.331	3.0
tristate	36	326.981	26.7
logic	74	384.505	31.4
physical_cells	0	0.000	0.0
total	152	1224.664	100.0

## Lab-5: Logic synthesis of an adding CPU

h) addingCPU \_quality\_created file

addingCPU_quality_created.rep				
Generated by: Genus(TM) Synthesis Solution 17.21-s010_1				
Generated on: May 04 2023 12:35:50 pm				
Module: AddingCPU				
Technology library: slow				
Operating conditions: slow (balanced_tree)				
Wireload mode: enclosed				
Area mode: timing library				
Timing				
-----				
Clock Period				
-----				
CLK_100M 10000.0				
-----				
Cost	Critical	Violating		
Group	Path Slack	TNS	Paths	
-----				
CLK_100M	6582.9	0.0	0	
default	No paths	0.0		
-----				
Total		0.0	0	
Instance Count				
-----				
Leaf Instance Count		152		
Physical Instance count		0		
Sequential Instance Count		24		
Combinational Instance Count		128		
Hierarchical Instance Count		6		
Area				
-----				
Cell Area		1224.664		
Physical Cell Area		0.000		
Total Cell Area (Cell+Physical)		1224.664		
Net Area		0.000		
Total Area (Cell+Physical+Net)		1224.664		
-----				
Max Fanout		20 (pc_on adr)		
Min Fanout		0 (dp/alu/b[7])		
Average Fanout		2.8		
Terms to net ratio		3.6345		
Terms to instance ratio		3.4671		
Runtime		15.096715 seconds		
Elapsed Runtime		197 seconds		
Genus peak memory usage		751.47		
Innovus peak memory usage		no value		
Hostname		cad20		

**Inference:** A total of 152 leaf instance count is present in the gate level netlist with total area of 1224.664, total power of 84068.804nW.

**Result:** Hence an addingCPU is synthesized and the gate level netlist with timing, area and power report has been generated.