

# Module 4

FSM and memory modelling

# Contents

- Synchronous and Asynchronous FIFO
- Single port and Dual port ROM and RAM
- FSM Verilog modeling of Sequence detector
- Serial adder
- Vending machine



# Synchronous FIFO

First In First Out (FIFO) is a very popular and useful design block for purpose of synchronization and a handshaking mechanism between the modules.

**Depth of FIFO:** The number of slots or rows in FIFO is called the depth of the FIFO.

**Width of FIFO:** The number of bits that can be stored in each slot or row is called the width of the FIFO.


There are two types of FIFOs

1. Synchronous FIFO
2. Asynchronous FIFO


 
# Synchronous FIFO

In Synchronous FIFO, data read and write operations use the same clock frequency. Usually, they are used with high clock frequency to support high-speed systems.



**Synchronous FIFO**

# Signals:

wr\_en: write enable

wr\_data: write data

full: FIFO is full

empty: FIFO is empty

rd\_en: read enable

rd\_data: read data

w\_ptr: write pointer

r\_ptr: read pointer



## **FIFO write operation**

FIFO can store/write the `wr_data` at every posedge of the clock based on `wr_en` signal till it is full. The write pointer gets incremented on every data write in FIFO memory.

## **FIFO read operation**

The data can be taken out or read from FIFO at every posedge of the clock based on the `rd_en` signal till it is empty. The read pointer gets incremented on every data read from FIFO memory.



The width of the write and read pointer =  $\log_2(\text{depth of FIFO})$ .

[Code Link](#)


The FIFO full and empty conditions can be determined as

### **Empty condition**

$w\_ptr == r\_ptr$  i.e. write and read pointers has the same value.
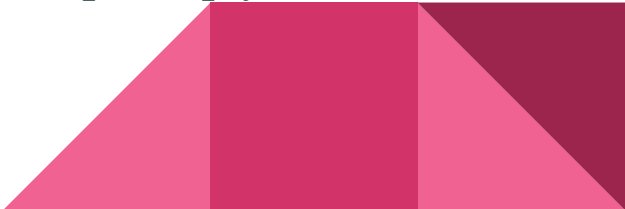
### **Full condition**

The full condition means every slot in the FIFO is occupied, but then  $w\_ptr$  and  $r\_ptr$  will again have the same value. Thus, it is not possible to determine whether it is a full or empty condition. Thus, the last slot of FIFO is intentionally kept empty, and the full condition can be written as  $(w\_ptr + 1 \text{ 'b' } 1) == r\_ptr$



 
# Asynchronous FIFO

- In asynchronous FIFO, data read and write operations use different clock frequencies.
- Usually, these are used in systems where data need to pass from one clock domain to another which is generally termed as ‘clock domain crossing’.
- Thus, asynchronous FIFO helps to synchronize data flow between two systems working on different clocks.








 
**Asynchronous FIFO**

## Asynchronous FIFO Operation

- In the case of asynchronous FIFO write pointer is aligned to the write clock domain whereas the read pointer is aligned to the read clock domain.
  - Hence, it requires domain crossing to calculate FIFO full and empty conditions.
  - This causes metastability in the actual design.
  - In order to resolve this metastability, 2 flip flops or 3 flip flops synchronizer can be used to pass write and read pointers.
- 

A single “2 FF synchronizer” can resolve metastability for only one bit.

Hence, depending on write and read pointers multiple 2FF synchronizers are required.



**2 flip-flop synchronizer**

# Usage of Gray codes

- Binary formatted write and read pointer values cannot be passed.
- Due to metastability, the overall write or read pointer value might be different.
- Both write and read pointers need to convert first to their equivalent gray code in their corresponding domain and then pass them to an opposite domain.



# Memory

- Read-only memory (ROM)
- Random Access Memory (RAM)
- Single port RAM
- Dual port RAM




# Single Port RAM

- A single-port RAM (Random Access Memory) is a type of digital memory component that allows data to be read from and written to a single memory location (address) at a time.
- It is a simple form of memory that provides a basic storage mechanism for digital systems.
- Each memory location in a single-port RAM can store a fixed number of bits (usually a power of 2, such as 8, 16, 32, etc.).




# Single Port RAM

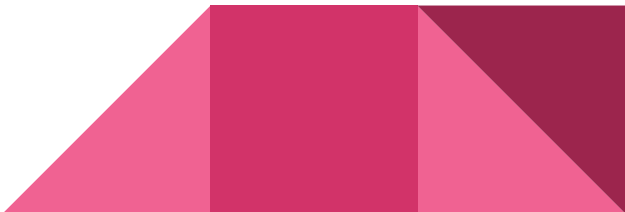- During a read operation, the data stored at a specific address is retrieved.
  - During a write operation, new data is stored at a specific address, replacing the previous data.
  - Single-port RAMs are commonly used in various digital systems for tasks such as data storage, temporary buffering, and data manipulation.
- 
 
# Signals

- Single-port RAMs have **address lines** that are used to select the memory location to be accessed. The number of address lines determines the maximum number of memory locations that the RAM can hold.
- **Data lines** are used to carry the actual data to be read from or written to the memory location.
- **Control signals**, such as read enable (read request) and write enable (write request), are used to initiate specific memory operations.





# Verilog Code

```
module single_port_ram(  
    input [7:0] data,      //input data  
    input [5:0] addr,      //address  
    input we,             //write enable  
    input clk,            //clk  
    output [7:0] q //output data  
);  
  
    reg [7:0] ram [63:0];      //8*64 bit ram  
    reg [5:0] addr_reg;  
                                //address register
```

```
    always @ (posedge clk)  
        begin  
            if(we)  
                ram[addr] <= data;  
            else  
                addr_reg <= addr;  
            end  
  
        assign q = ram[addr_reg];  
  
endmodule
```

```

module single_port_ram_tb;
    reg [7:0] data;          //input data
    reg [5:0] addr;          //address
    reg we;                  //write enable
    reg clk;                 //clk
    wire [7:0] q;            //output data

```

```

    single_port_ram spr1(
        .data(data),
        .addr(addr),
        .we(we),
        .clk(clk),
        .q(q)
    );

```

```

    initial
    begin
        $dumpfile("dump.vcd");
        $dumpvars(1, single_port_ram_tb);

        clk=1'b1;
        forever #5 clk = ~clk;
    end

```

```

    initial
    begin

```

```
        we = 1'b1;

```

```
        data = 8'h01;

```

```
        addr = 5'd0;

```

```
        #10;

```

```
        data = 8'h02;

```

```
        addr = 5'd1;

```

```
        #10;

```

```
        data = 8'h03;

```

```
        addr = 5'd2;

```

```
        #10;

```

```
        addr = 5'd0;

```

```
        we = 1'b0;

```

```
        #10;

```

```
        addr = 5'd1;

```

```
        #10;

```

```
    end

```


```
endmodule

```

# Dual Port RAM

- Possible to access the same address locations through two ports.
- The various modes of a typical true dual port RAM is shown below.

modes	ena	wea	enb	web	portA	portB
1	1	1	1	1	write	write
2	1	1	1	0	write	read
3	1	0	1	1	read	write
4	1	0	1	0	read	read

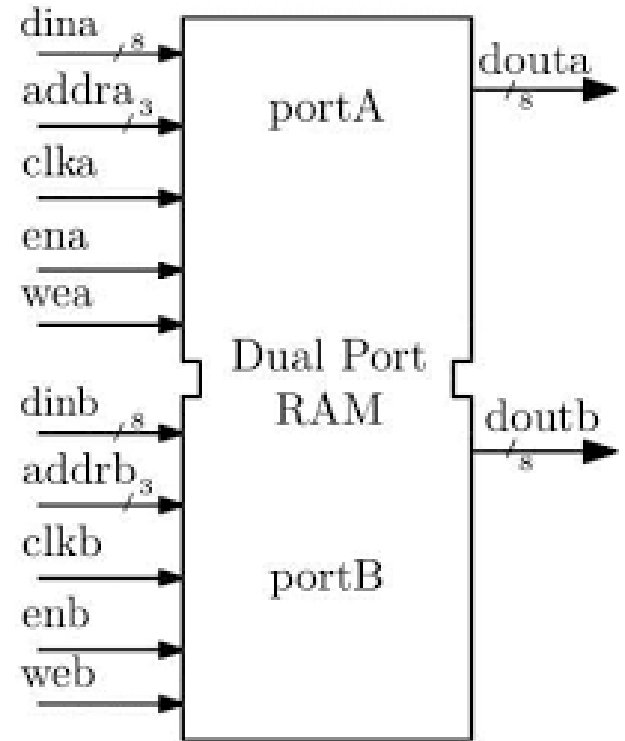

```
module dp_ram (  
  clka,clkb,  
  ada,adb,  
  ina,inb,  
  ena,enb,  
  wea,web,  
  outa,outb);  
  
  input clka,clkb,ena,wea,enb,web;  
  input[2:0] ada,adb;  
  input[7:0] ina,inb;  
  
  output reg [7:0] outa,outb;  
  
  reg [7:0] mem [0:7];  
  
  initial begin  
    outa = 8'b00000000;  
    outb = 8'b00000000;  
  end
```

```
    always@(posedge clka)  
      if(ena)  
        begin  
          if(wea)  
            mem[ada]=ina;  
          else  
            outa = mem[ada];  
          end  
        else  
          outa = outa;  
        always@(posedge clkb)  
          if(enb)  
            begin  
              if(web)  
                mem[adb]=inb;  
              else  
                outb = mem[adb];  
              end  
            else  
              outb = outb;  
          endmodule
```


# SEQUENCE DETECTOR

- A sequence detector is a sequential state machine that takes an input string of bits and generates an output 1 whenever the target sequence has been detected.
- In a Mealy machine, output depends on the present state and the external input ( $x$ ).
- Sequence detector is of two types:
  - Overlapping
  - Non-Overlapping
- In an overlapping sequence detector, the last bit of one sequence becomes the first bit of the next sequence.
- In a non-overlapping sequence detector, the last bit of one sequence does not become the first bit of the next sequence.


 
# Example

- Design a FSM which detects the sequence “1011” from a given bit stream. Explain with neat state diagram for overlapping case.
- State Diagram



# Verilog Code

```
module sd1011_mealy_over(
    input bit clk,
    input logic reset,
    input logic din,
    output logic dout);

    typedef enum logic [1:0]{S0, S1, S2, S3}
    state_t;
    state_t state;

    always @(posedge clk or posedge reset)
    begin
        if(reset) begin
            dout <= 1'b0;
            state <= S0;
        end
        else begin
            case(state)
```

```
            S0: begin
                if(din) begin
                    state <= S1;
                    dout <= 1'b0;
                end
                else
                    dout <= 1'b0;
            end
            S1: begin
                if(~din) begin
                    state <= S2;
                    dout <= 1'b0;
                end
                else begin
                    dout <= 1'b0;
                end
            end
        end
```

```
            S2: begin
                if(~din) begin
                    state <= S0;
                    dout <= 1'b0;
                end
                else begin
                    state <= S3;
                    dout <= 1'b0;
                end
            end
            S3: begin
                if(din) begin
                    state <= S1;
                    dout <= 1'b1;
                end
                else begin
                    state <= S2;
                    dout <= 1'b0;
                end
            end
        endcase
    end
end endmodule
```

# Vending Machine

- Newspaper vending machine.
- In this vending machine, it accepts only two coins, 5 point and 10 point. Whenever total of coins equal to 15 points, then nw\_pa signal will go high and user will get news paper. It will not return any coin, if total of points exceeds 15 points.
- System Specification:

Sr. No.	Name of the Pin	Direction	Width	Description
1	Nw_pa	Output	1	News Paper Signal
2	Coin	Input	2	Only two Coins, 5 =2'b01 10 =2'b10 0 =2'b00
3	Clk	Input	1	Clock Signal
4	Rst	Input	1	Reset Signal



```

module vending_machine
    (nw_pa,clk,coin,rst);
output reg nw_pa;
input [1:0] coin;
input clk,rst; reg [1:0] state;
reg [1:0] next_state;

parameter [1:0] s0=2'b00;
parameter [1:0] s5=2'b01;
parameter [1:0] s10=2'b10;
parameter [1:0] s15=2'b11;

always @(posedge clk)
begin
    if (rst)
        state=s0;
    else
        state=next_state;
end

```

```

always @(state,coin)
begin
    case (state)
s0: begin
    if (coin==2'b00)
        next_state=s0;
    else if (coin==2'b01)
        next_state=s5;
    else if (coin==2'b10)
        next_state=s10;
end
s5: begin
    if (coin==2'b00)
        next_state=s5;
    else if (coin==2'b01)
        next_state=s10;
    else if (coin==2'b10)
        next_state=s15;
end

```

```

s10: begin
if (coin==2'b00)
    next_state=s10;
else if (coin==2'b01)
    next_state=s15;
else if (coin==2'b10)
    next_state=s15;
end
s15: begin
    next_state=s0;
end
default : next_state=s0;
endcase end
always @(state)
begin
    case (state)
s0 : nw_pa<=1'b0;
s5 : nw_pa<=1'b0;
s10: nw_pa<=1'b0;
s15: nw_pa<=1'b1;
default: nw_pa<=1'b0; endcase end
endmodule

```