

Module – 3


Implementation of Arithmetic system

Contents

- Arithmetic Circuits:
 - High Speed Adders,
 - Carry look-ahead adder,
 - Carry save adders,
 - Conditional Sum adders,
 - Sequential and Parallel Multipliers
-

Ripple Carry Adder

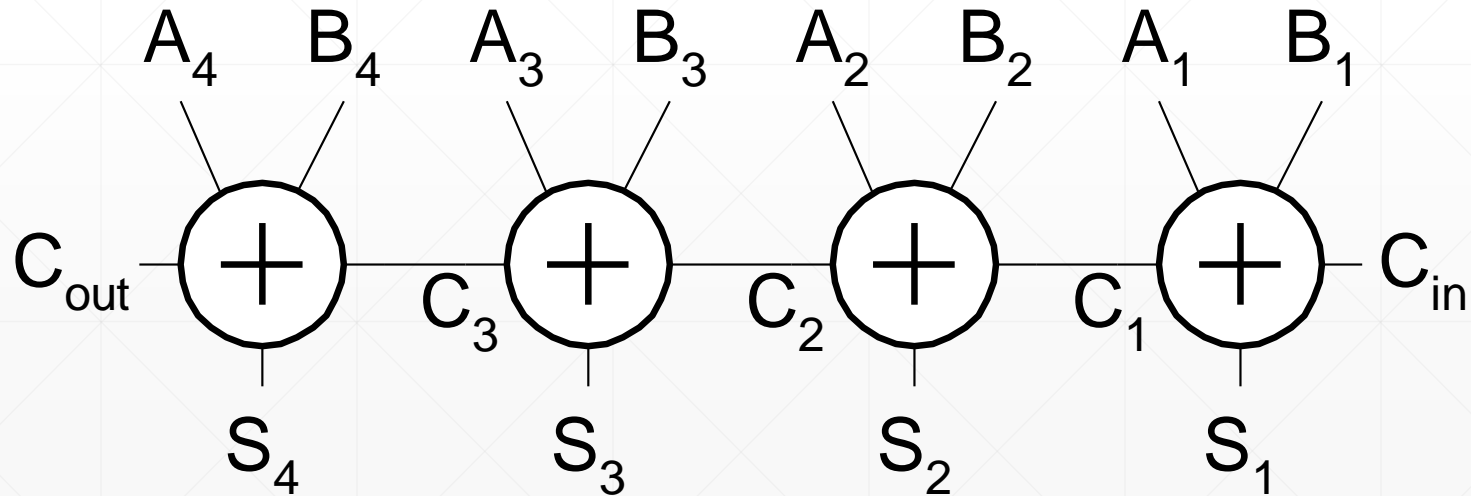
- Simplest design: cascade full adders
 - Critical path goes from C_{in} to C_{out}
 - Design full adder to have fast carry delay



Ripple Carry Adder

✓ Critical Delay

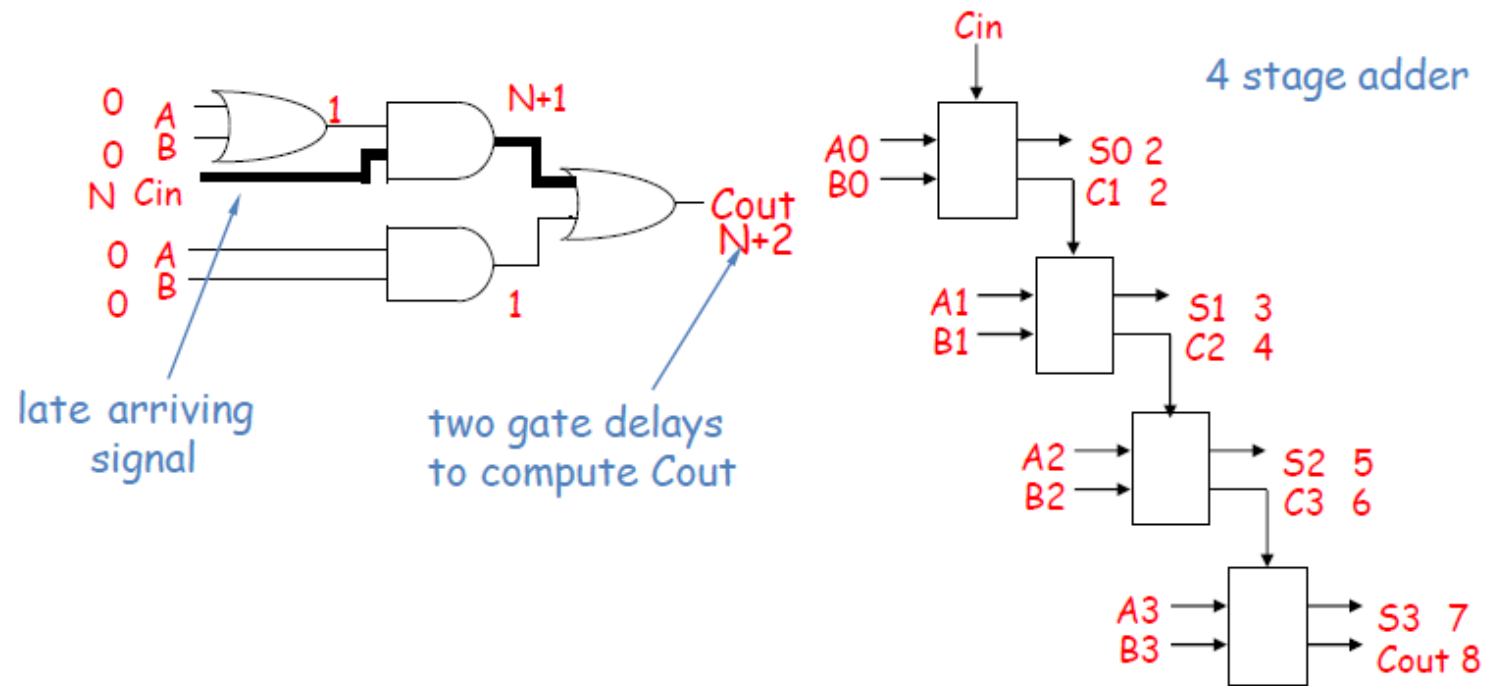- The propagation of carry from low to high order stages



Carry Look-ahead Adder

- Express Sum and Carry as a function of P, G, D.

$$\text{Generate (G)} = AB$$

$$\text{Propagate (P)} = A \oplus B$$

$$\text{Delete} = \overline{A} \overline{B}$$

- Derive expressions for S and Co based on G and P

$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$

Carry Look-ahead Adder

Therefore:

$$C_1 = G_1 + P_1 C_0$$


$$C_2 = G_2 + P_2 (G_1 + P_1 C_0)$$

$$C_3 = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 C_0))$$

$$C_4 = G_4 + P_4 (G_3 + P_3 (G_2 + P_2 (G_1 + P_1 C_0)))$$

- Expanded formula does not depend on intermediate carries.
 - Allows carry for each bit to be computed independently.
-


Depth-4 carry-lookahead

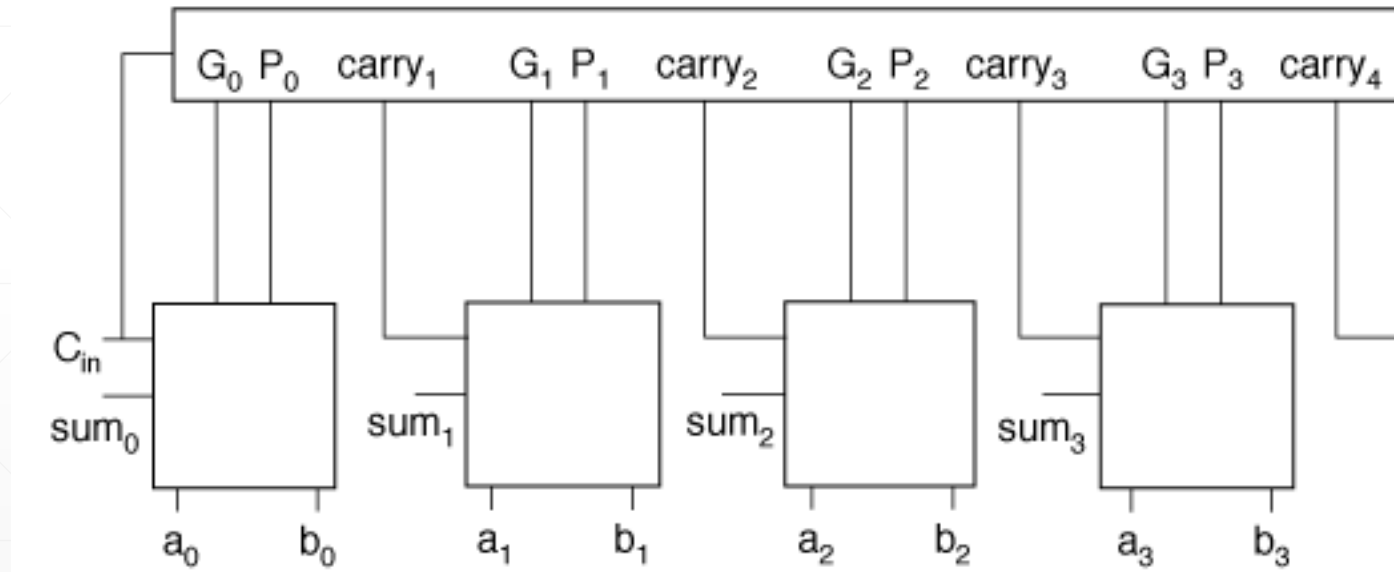


Carry Save Adders

- A carry-save adder or CSA is a type of digital adder mainly used for computing the sum of a minimum of three or above binary numbers very efficiently.
 - A CSA is normally used within a binary multiplier because this multiplier involves the addition of the above two binary numbers after multiplication.
 - By using this method, a big adder can be implemented which is very faster compared to the usual addition of numbers.
-

Carry Save Adder

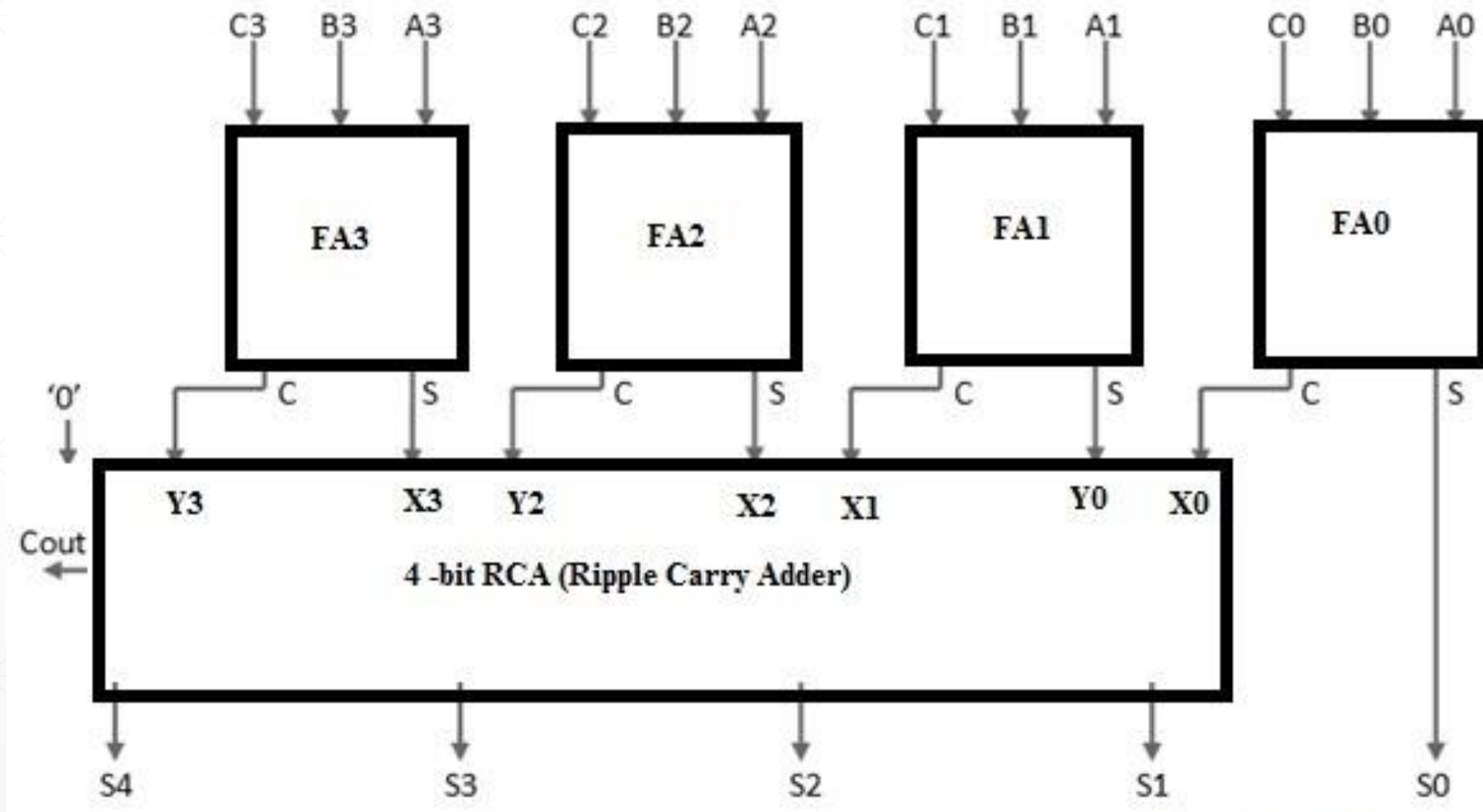

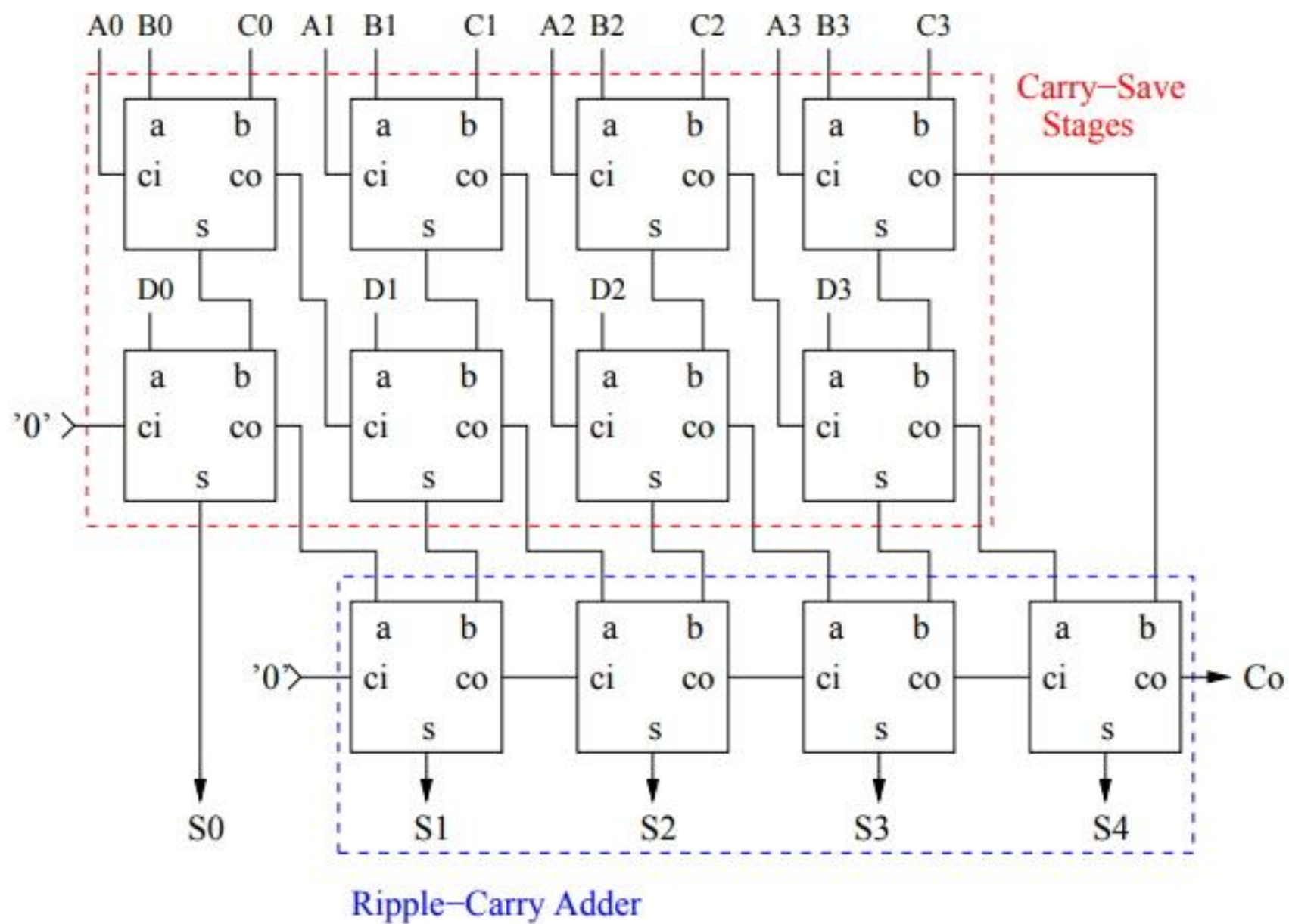


Carry-skip adder

- A carry-skip adder (also known as a carry-bypass adder) is an adder implementation that improves on the delay of a ripple-carry adder with little effort compared to other adders.
 - The improvement of the worst-case delay is achieved by using several carry-skip adders to form a block-carry-skip adder.
 - Unlike other fast adders, carry-skip adder performance is increased with only some of the combinations of input bits. This means, speed improvement is only probabilistic.
-


Carry-skip adder

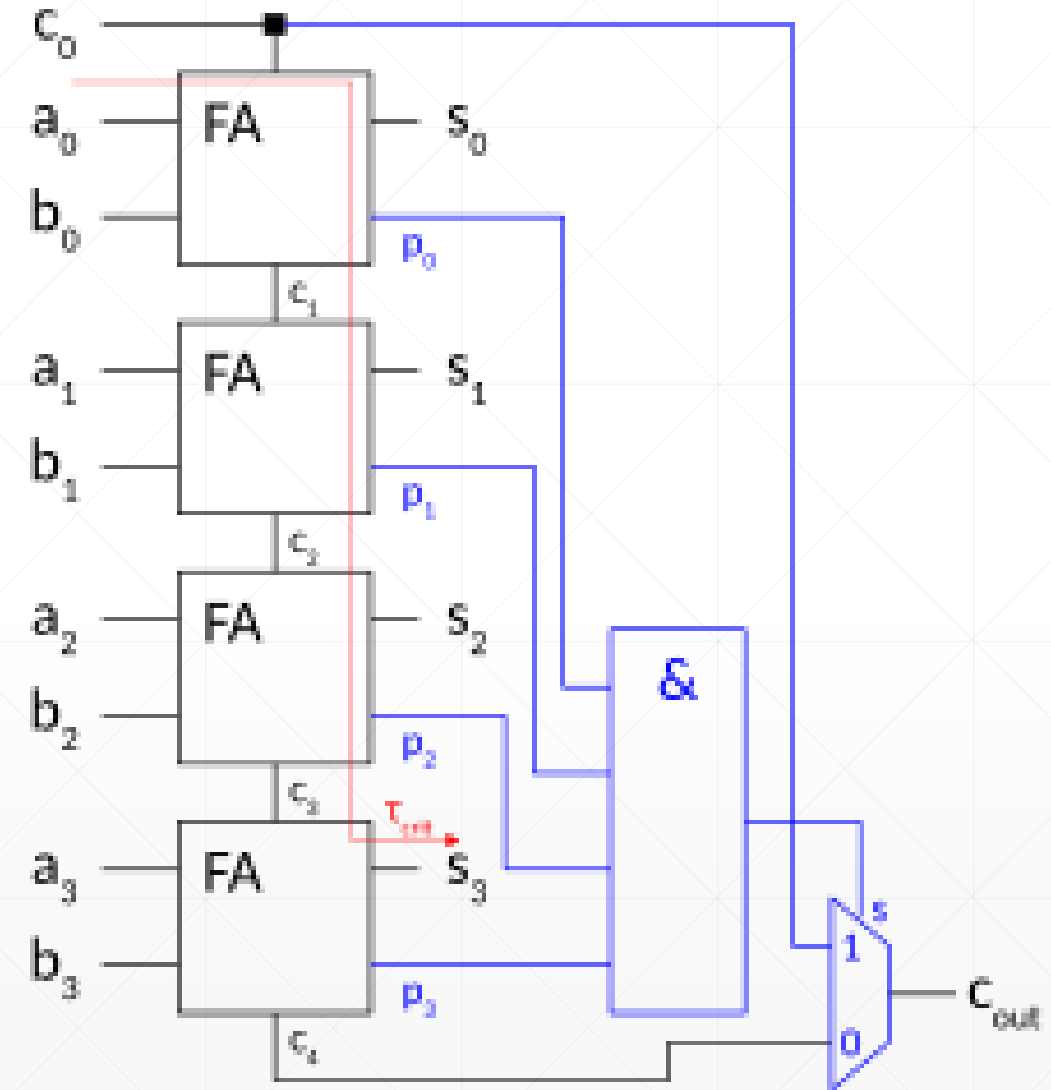- The n-bit-carry-skip adder consists of a n-bit-carry-ripple-chain, a n-input AND-gate and one multiplexer.
- Each propagate bit p_i , that is provided by the carry-ripple-chain is connected to the n-input AND-gate.
- The resulting bit is used as the select bit of a multiplexer that switches either the last carry-bit c_n or the carry-in c_0 to the carry-out signal c_{out}



Carry Select Adder


- The carry-select adder generally consists of ripple-carry adders and a multiplexer.
- Adding two n -bit numbers with a carry-select adder is done with two adders (therefore two ripple-carry adders), in order to perform the calculation twice, one time with the assumption of the carry-in being zero and the other assuming it will be one.
- After the two results are calculated, the correct sum, as well as the correct carry-out, is then selected with the multiplexer once the correct carry-in is known.

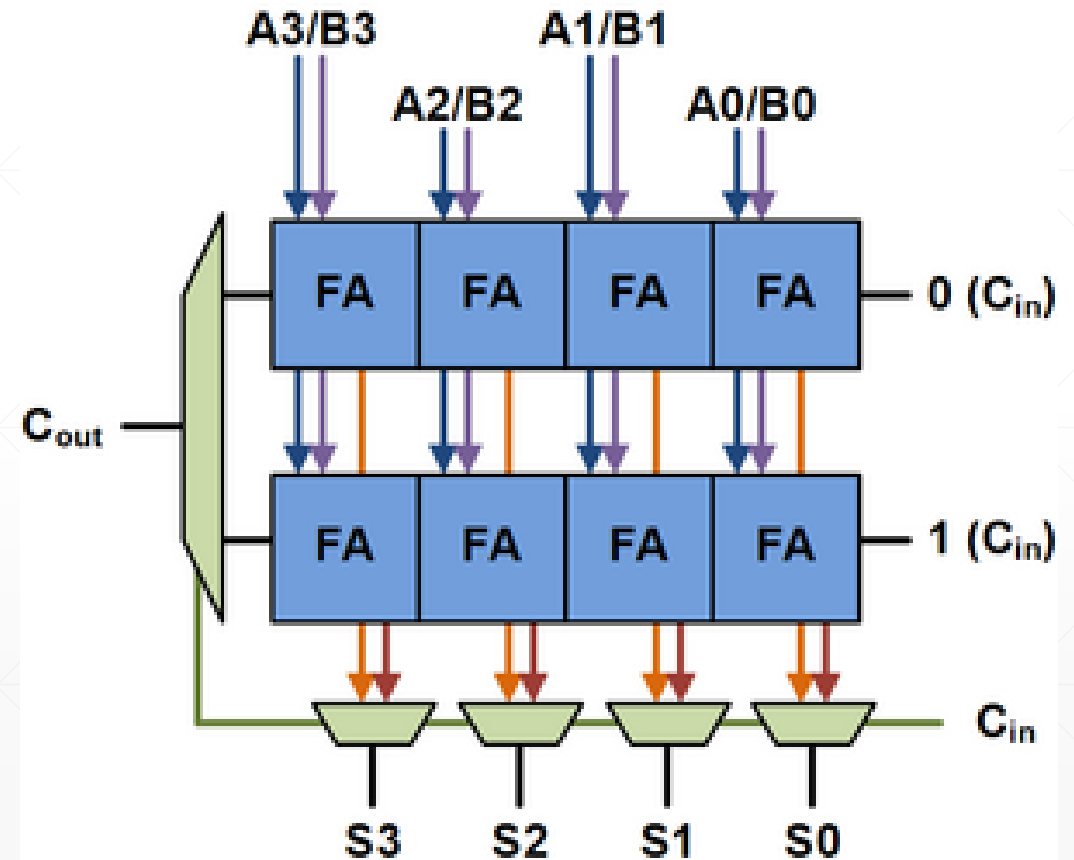


Carry Select Adder

- The number of bits in each carry select block can be uniform, or variable.

Uniform-sized adder

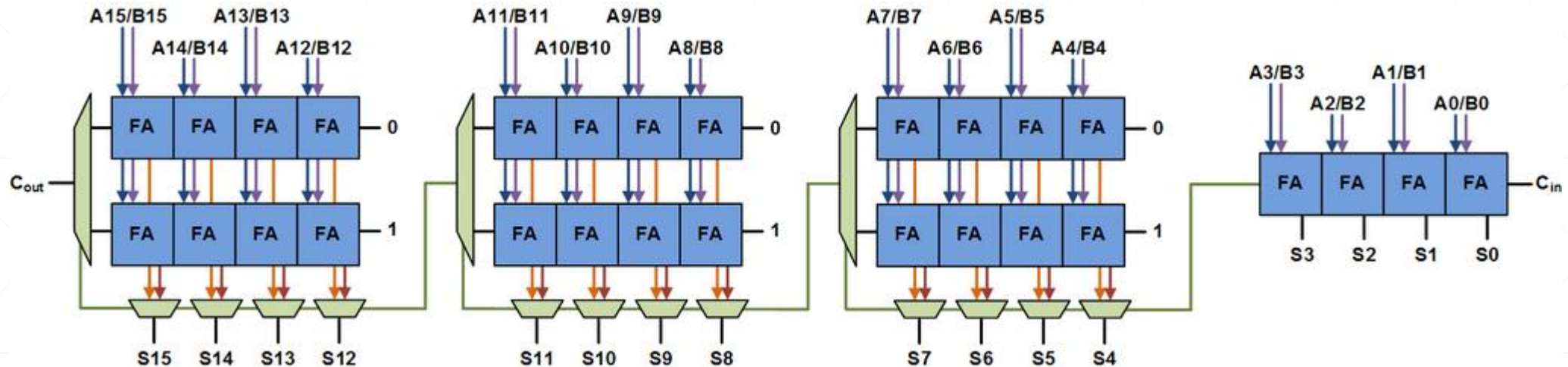

Variable-sized adder

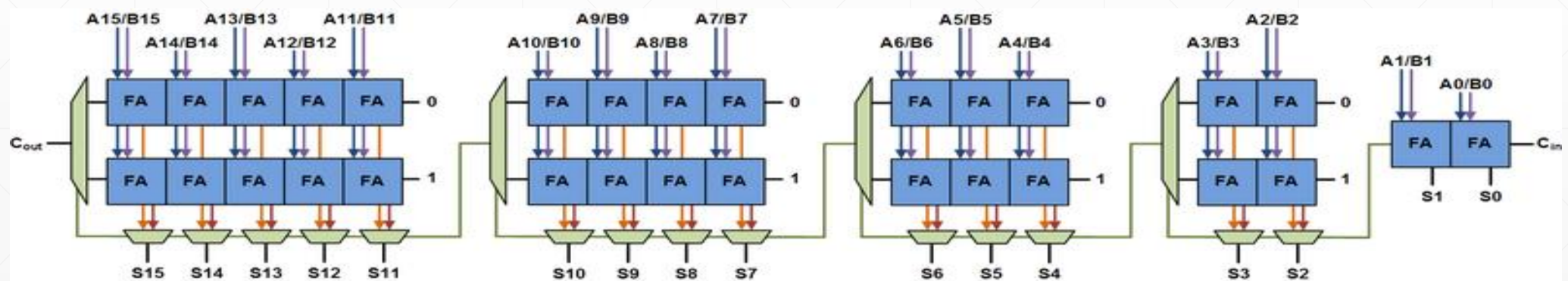

Conditional Sum Adder

- Extension of carry-select adder
- Carry select adder
- One-level using $k/2$ -bit adders
- Two-level using $k/4$ -bit adders
- Three-level using $k/8$ -bit adders
- Assuming k is a power of two, eventually have an extreme where there are $\log_2 k$ -levels using 1-bit adders

